

Practical No: 5

Aim: To study and verify Thevenin's Theorem.

AIM: To Study and verify Thevenin's Theorem

APPARATUS:

1. Network Theorems Trainerkit.
2. Multimeter.
3. Connecting Leads.


THEORETICAL BACKGROUND:

Thevenin Theorem is converse of Norton's Theorem. It consists of equivalent current source instead of equivalent voltage source as we do in Norton's theorem. The determination of internal resistance of the source network is identical in both the theorems. However, in final stage, i.e., in the Thevenin equivalent circuit, the equivalent voltage source is placed in series with the internal resistance unlike to that in Norton's theorem where the current generator was placed in parallel to the internal resistance

Statement of Thevenin's Theorem :

A linear active network consisting of independent and dependent voltage and current sources and linear bilateral network elements can be replaced by an equivalent circuit, consisting of a voltage source in series with a resistance. The voltage source being the open circuited voltage across the load terminal and the resistance being the internal resistance of the source network, looking through the open circuited load terminals.

PROCEDURE:

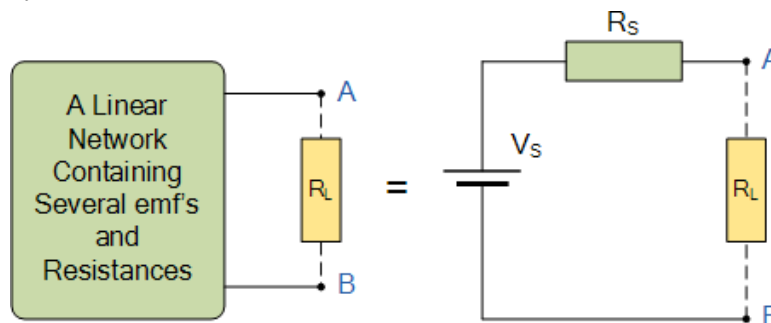

Sequences to find value of R_{TH} and V_{TH}

1. Remove that portion of the network across which the Thevenin equivalent circuit is to be found. In the figure 1, this requires that the load resistor R_L be temporarily removed from the network.

2. R_{TH}

Calculate R_N by first setting all sources to zero (voltage sources are replaced by short circuits and current sources by open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.)

$$R_N = R_3 + (R_1 R_2 / R_1 + R_2)$$

3. V_{TH}

Calculate V_{TH} by first open the load and find the open circuit voltage across the load terminals using conventional network analysis.


$$V_{TH} = (E / R_1 + R_2) R_2$$

Thevenin's equivalent circuit is drawn by keeping R_N in series to voltage source as shown in figure1.

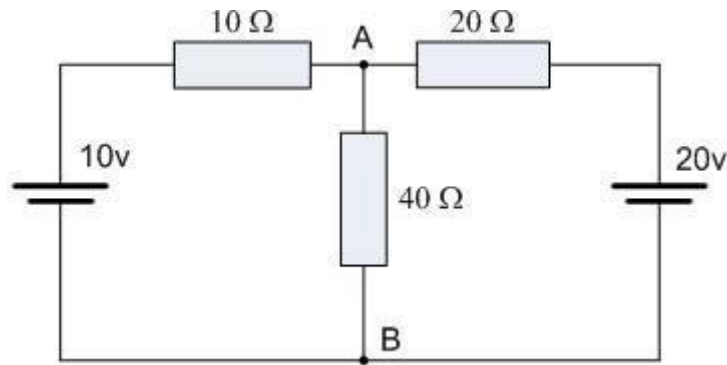
4. Reconnect the load resistance (R_L) across the load terminal and the current through it (I_L) is then givenby;

$$I_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)$$

For example, consider the following circuit;



Firstly, we have to remove the centre 40Ω resistor and short out (not physically as this would be dangerous) all the emf's connected to the circuit, or open circuit any current sources. The value of resistor R_s is found by calculating the total resistance at the terminals A and B with all the emf's removed, and the value of the voltage required V_s is the total voltage across terminals A and B with an open circuit and no load resistor R_s connected. Then, we get the following circuit;

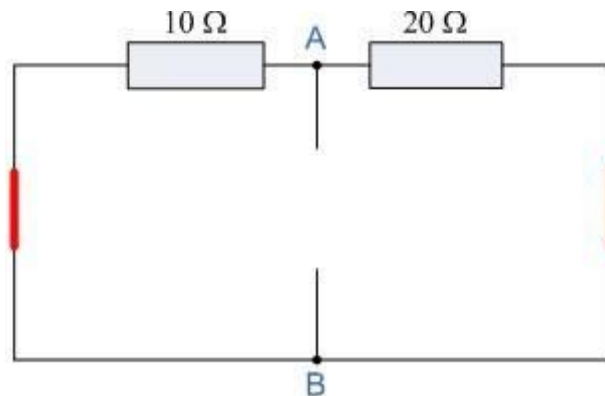


Find the Equivalent Resistance (R_s):

10Ω Resistor in parallel with the 20Ω Resistor

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 10}{20 + 10} = 6.67\Omega$$

Find the Equivalent Voltage (V_s):

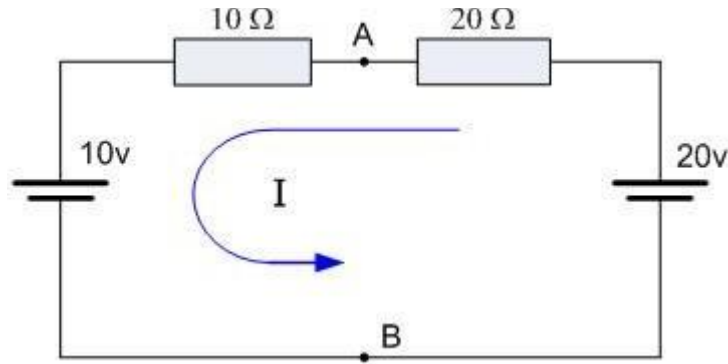


We now need to reconnect the two voltages back into the circuit, and as $V_S = V_{AB}$ the current flowing around the loop is calculated as:

$$I = \frac{20v - 10v}{20\Omega + 10\Omega} = 0.33\text{amps}$$

So the voltage drop across the 20Ω resistor can be calculated as:

$$V_{AB} = 20 - (20\Omega \times 0.33\text{amps}) = 13.33 \text{ volts.}$$

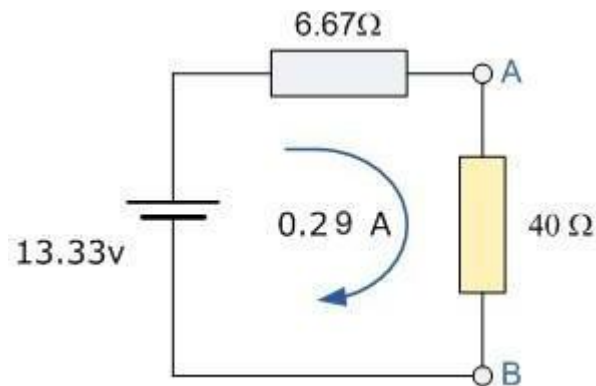Then the Thevenin's Equivalent circuit is shown below with the 40Ω resistor connected.




And from this the current flowing in the circuit is given as:

$$I = \frac{13.33v}{6.67\Omega + 40\Omega} = 0.29\text{amps}$$


Thevenin's theorem can be used as a circuit analysis method and is particularly useful if the load is to take a series of different values. It is not as powerful as Mesh or Nodal analysis in larger networks because the use of Mesh or Nodal analysis is usually necessary in any Thevenin exercise, so it might well be used from the start. However, Thevenin's equivalent circuits of Transistors, Voltage Sources such as batteries etc, are very useful in circuit design.

Verification of Thevenin's Theorem using the virtual lab simulator:


virtual lab:

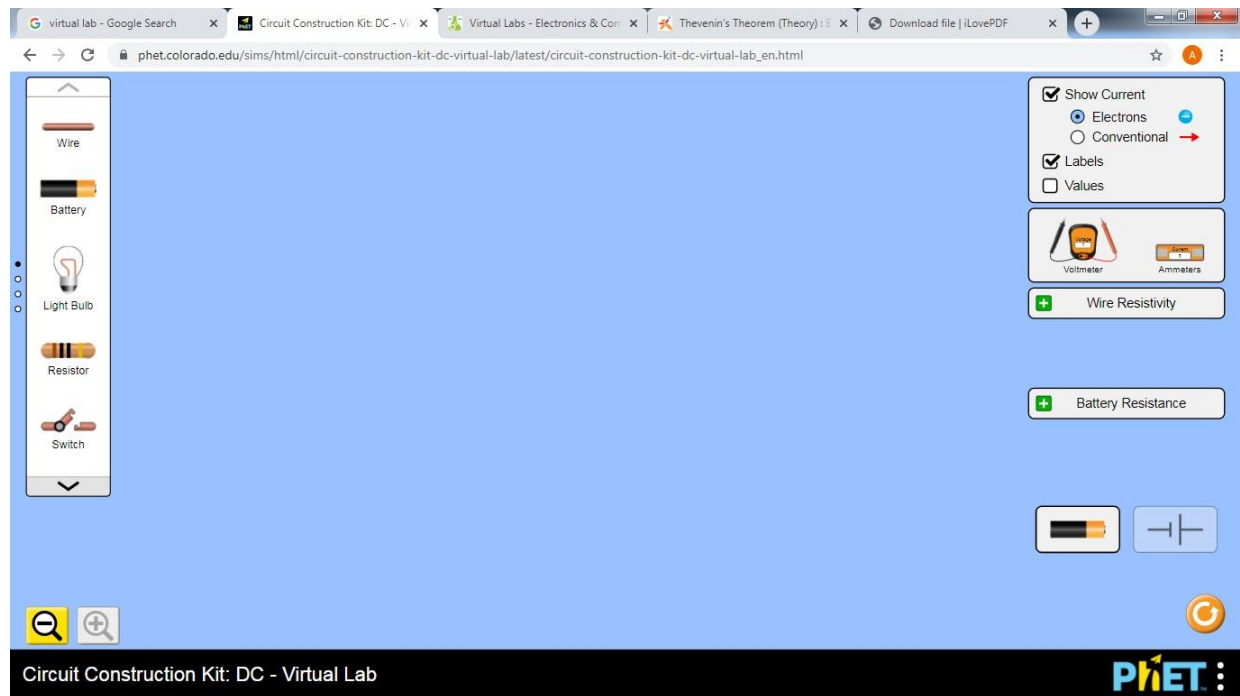

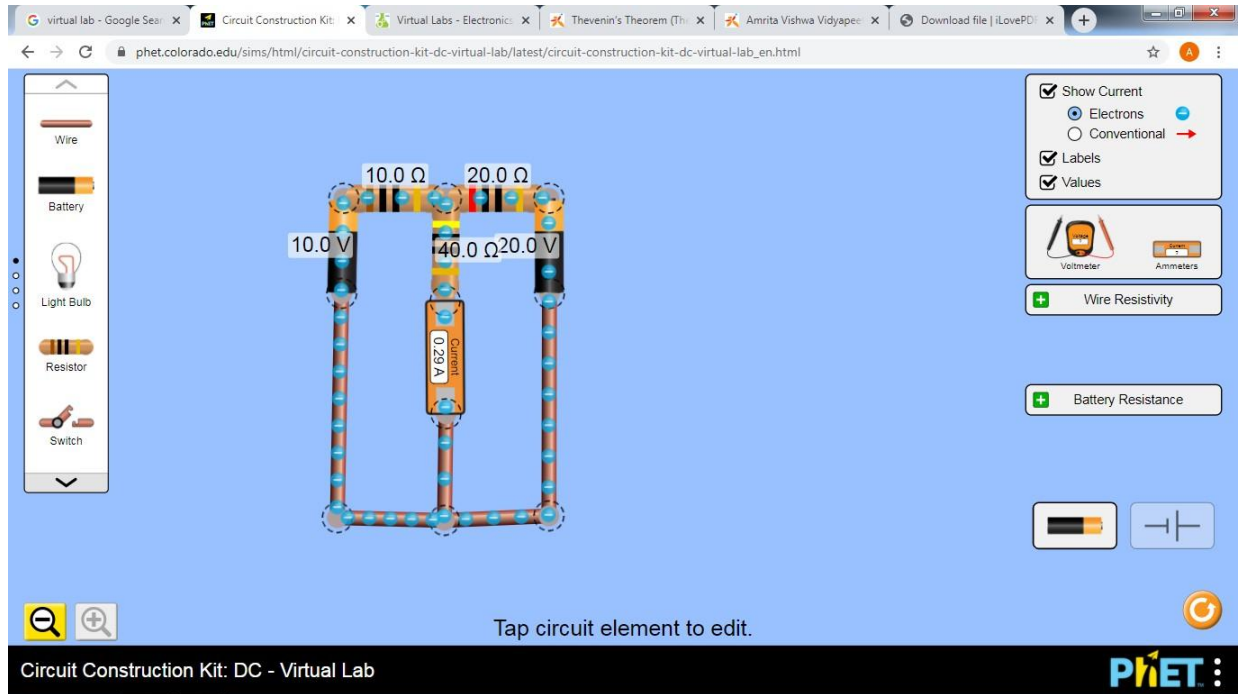step1 :- Create the actual circuit and measure the current across the load points .



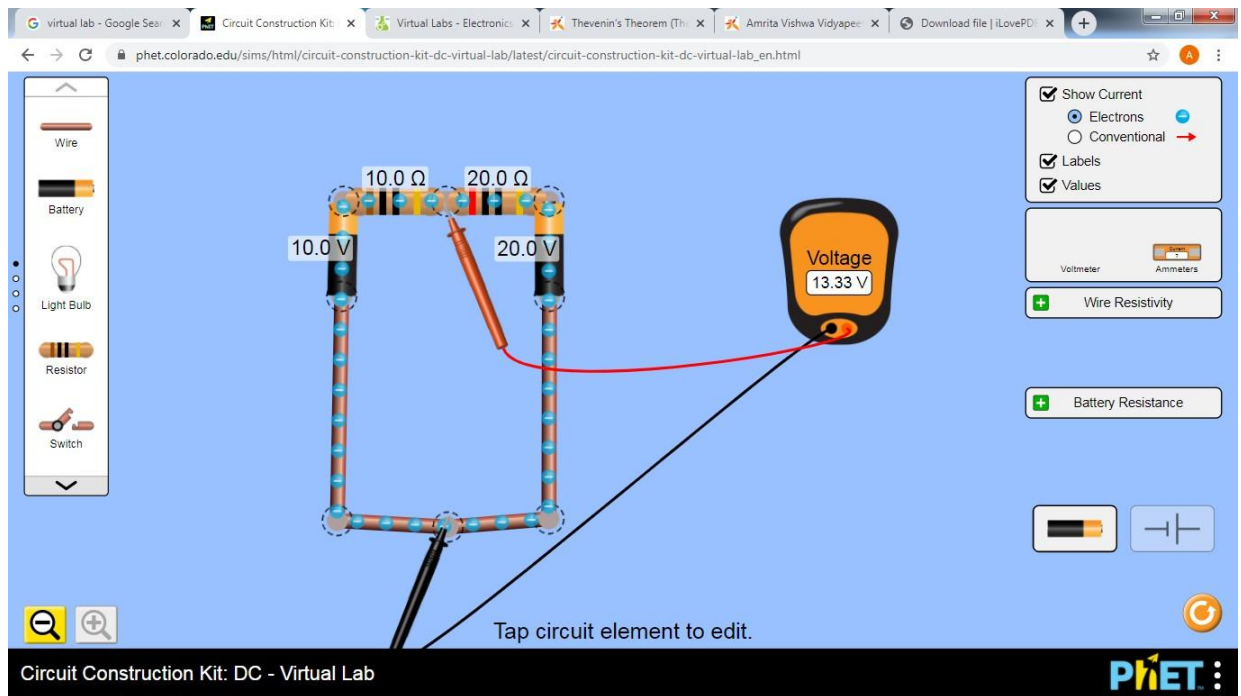Step 2 :- create the voltage across load 40 ohm by this simulator,



Step 3 :- Create the loop current according to KVL as per in theory in page 11 for find V_{TH} .

The screenshot shows the PhET Circuit Construction Kit: DC - Virtual Lab interface. The circuit is a single loop with a 10.0 V battery on the left, a 10.0 Ω resistor on the top, a 20.0 Ω resistor on the right, and a 20.0 V battery on the bottom. An ammeter in the bottom wire shows a current of 0.33 A. The interface includes a component palette on the left, a settings panel on the right, and a PhET logo at the bottom right.

Component Palette (Left):

- Wire
- Battery
- Light Bulb
- Resistor
- Switch

Settings Panel (Right):

- ☒ Show Current
 - ☐ Electrons
 - ☒ Conventional
- ☒ Labels
- ☒ Values
- Voltmeter
- Ammeters
- Wire Resistivity
- Battery Resistance


Bottom Bar:

Circuit Construction Kit: DC - Virtual Lab

PhET

Step4:-Create the Thevenin's equivalent circuit

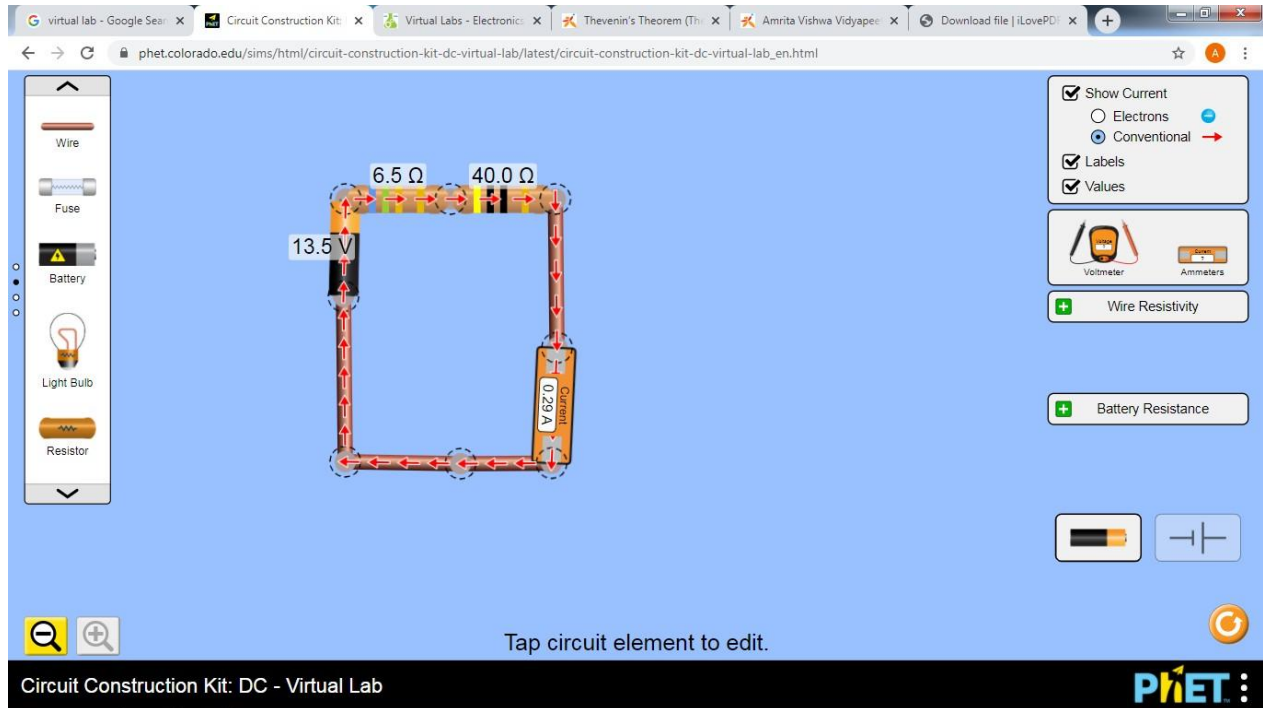by first creating the equivalent voltage source and equivalent resistance and then measure the current across the load using an ammeter.



RESULT TABLE:

Sr. No		V_{TH} (v)	R_{TH} (ohm)	I_L (A)
1	Theoretically	13.33	6.67	0.29
2	Practically	13.33	6.67	0.2856

CONCLUSION: