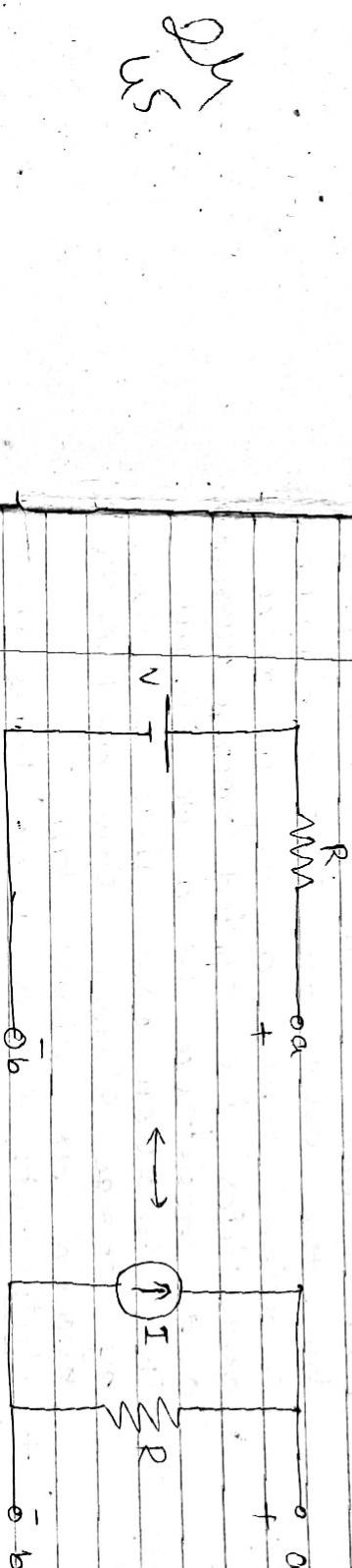


Ch. 1 D.C. Circuits

* Source Transformation:

\Rightarrow A Voltage Source with a series resistance can be converted into an equivalent current source with a parallel resistance.



(a)

\Rightarrow Conversely, a current source with a parallel resistance can be converted into a voltage source with a series resistance.

\Rightarrow Source conversion can be applied to controlled source as well. The controlling variable, however, must not be transposed with any other since the operation at the controlled source depends on it.

(b)

* Ohm's Law:-

\Rightarrow As the rate of flow of water through a pipe is directly proportional to the effective pressure and inversely

proportional to the frictional resistance similarly the current flowing through a conductor is directly proportional to the potential difference across the ends of the conductor and inversely proportional to the resistance offered by the conductor. Thus a definite relation exists among the three quantities i.e. applied voltage, current and resistance in a dc circuit.

This relation was first discovered by George Simon Ohm, and it is known as Ohm's law.
Statement: Ohm's law states that the current flowing between two points of a conductor is directly proportional to the potential difference across them, provided the physical conditions do not change.

\Rightarrow Mathematically,

$$I \propto V \text{ or } \frac{V}{I} = \text{constant}$$

$$\text{or } \frac{V_1}{I_1} = \frac{V_2}{I_2} = \dots = \frac{V_n}{I_n} = \text{constant.}$$

\Rightarrow In other words Ohm's law can also be stated as:
 The ratio of potential difference across any two points of a conductor is equal to the current flowing between them.

It can also be stated as $V = IR$ or $I = V/R$

* Limitations:-

1) Ohm's law does not apply to all non-metallic conductors.


2) It also does not apply to non-linear devices such as zener diode.

3) It is true for metal conductors at constant temperature. If the temperature changes, the law is not applicable.

* Temp. co-efficient of Resistance:-

The resistance of most electrical conductors with the change in temperature is true. The resistance of a pure metallic conductor increases with increase in temperature and decrease with decrease in temperature. The variation of resistance with temperature is governed by a property of the material called the temp. co-efficient of resistance.

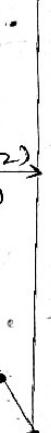⇒ If the resistance at any pure metal is plotted on a temp. base R_t is found that over the normal range of temperatures, the graph is practically a straight line.



above eqⁿ provided that to see that particular material is known.

⇒ Let a metallic conductor having a resistance of R_0 at 0°C be heated to $t^\circ\text{C}$ and let R_t be resistance at this temp. be R_t .

$$From \text{ eqn } (1), we \text{ have}$$

$$R_t = \frac{t_0 + t}{t_0} R_0$$

$$\Rightarrow R_t = \left(\frac{t_0 + t}{t_0} \right) R_0$$

$$= \left(1 + \frac{t}{t_0} \right) R_0 = R_0 + \frac{1}{R_0} t$$

$$\therefore R_t - R_0 = \frac{1}{R_0} t \quad (2)$$

$$\Rightarrow change \text{ in resistance, } \Delta R = R_t - R_0$$

$$= \frac{1}{R_0} R_0 t$$

$$= R_0 t \quad (3)$$

where $\alpha_0 = \frac{1}{R_0}$ is called the temp. coefficient of resi. of the material at 0°C . The eqⁿ (3) may be written as

$$\Delta R = \alpha_0 R_0 t \quad (4)$$

⇒ whence R_t and R_{t_1} are the resistances at temperatures t and t_1 respectively. Thus, if the resistance R_t , for any temperature t is known, then resistance for any other temp. t_1 can be calculated from eqⁿ (3).

Computation of resistance at diff. temp.

⇒ (1) If R_0 and α_0 are given, then the resistance R_t at any other temp.

from eqⁿ (3)

$$\Delta R = R_t - R_o = \alpha_o R_o t.$$

$$\therefore R_t = R_o + \alpha_o R_o t = R_o [1 + \alpha_o t] \quad \text{--- (4)}$$

(P.P) In case R_o is not given but α_o is given, then relation betⁿ the known resistance R_{t_1} at $t_1^{\circ}\text{C}$ and the un-known resistance R_{t_2} at $t_2^{\circ}\text{C}$ can be found as follows:

\Rightarrow Eqⁿ (4) can be rearranged as

$$R_{t_1} = R_o [1 + \alpha_o t_1] \quad \text{--- (5),}$$

$$R_{t_2} = R_o [1 + \alpha_o t_2] \quad \text{--- (6)}$$

\Rightarrow Taking the ratio of the eqⁿs (5) & (6)

$$\frac{R_{t_2}}{R_{t_1}} = \frac{R_o [1 + \alpha_o t_2]}{R_o [1 + \alpha_o t_1]} = \frac{1 + \alpha_o t_2}{1 + \alpha_o t_1}$$

$$\text{Thus, } \frac{R_{t_2}}{R_{t_1}} = \frac{1 + \alpha_o t_2}{1 + \alpha_o t_1} \quad \text{--- (#)}$$

$$\text{or } \frac{R_{t_2}}{R_{t_1}} = [(1 + \alpha_o t_2)(1 + \alpha_o t_1)]^{-1}$$

$$\stackrel{(2)}{=} (1 + \alpha_o t_2)(1 - \alpha_o t_1)$$

$$\stackrel{(3)}{=} 1 + \alpha_o t_2 - \alpha_o t_1 - \alpha_o^2 t_1 t_2$$

$$\stackrel{(4)}{=} 1 + \alpha_o (t_2 - t_1) \quad \text{--- (7).}$$

$$\text{or } R_{t_2} = R_{t_1} [1 + \alpha_o (t_2 - t_1)] \quad \text{--- (8).}$$

* Computation of a unkⁿ diff. tempⁱ:

C.P) Relation betⁿ α_o and α_{t_1} :-

\Rightarrow consider a conductor of resistance

R_o at 0°C . When pts temp. is raised to $t_1^{\circ}\text{C}$ its res. increases to R_{t_1} .

$$R_{t_1} = R_o [1 + \alpha_o t_1] \quad \text{--- (1)}$$

\Rightarrow Let us suppose that the conductor or resistance R_{t_1} at $t_1^{\circ}\text{C}$ be now cooled down to 0°C to give a resistance of the value R_o .

$$\text{Then, } R_o = R_{t_1} [1 + \alpha_{t_1} (0 - t_1)] \quad \text{--- (2).}$$

$$\text{From eqⁿ (1),}$$

$$R_o = R_{t_1} - R_{t_1} \cdot \alpha_{t_1} \cdot t_1 \quad \text{--- (3)}$$

$$\text{or } \alpha_{t_1} = \frac{R_{t_1} - R_o}{t_1 \times R_{t_1}} \quad \text{--- (4)}$$

Substituting the value of R_{t_1} from eqⁿ (1) we get $\alpha_{t_1} = \frac{R_o + R_o \alpha_{t_1} - R_o}{t_1 \times R_o [1 + \alpha_{t_1}] - R_o}$

$$= \frac{\alpha_o}{1 + \alpha_o t_1} \quad \text{--- (5)}$$

(P.P) Relation betⁿ α_{t_1} and α_{t_2} :-

$$\Rightarrow \text{From eqⁿ (4), } \alpha_{t_1} = \frac{\alpha_o}{1 + \alpha_o t_1}$$

\Rightarrow Similarly, if the final temp. is $t_2^{\circ}\text{C}$ and the corresponding value of α is α_{t_2} then $\alpha_{t_2} = \frac{\alpha_o}{1 + \alpha_o t_2} \quad \text{--- (6)}$

$$\Rightarrow \text{From eqⁿs (4) & (5),}$$

$$\frac{1}{\alpha_{t_2}} - \frac{1}{\alpha_{t_1}} = \frac{1 + \alpha_o t_2}{\alpha_o} - \frac{1 + \alpha_o t_1}{\alpha_o}$$


$$\alpha_{t_2} = \frac{1}{t_2} + (t_2 - t_1)$$

$$\text{or } \alpha_{t_2} = \frac{1}{(t_2 - t_1)}$$

$$\frac{1}{t_2} = \frac{1}{t_1} + (t_2 - t_1)$$

Resistance in series:-

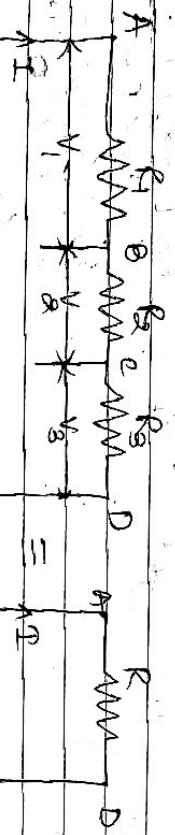When resistors are connected end to end, so that they form one path for the flow of current, then resistors are said to be connected in series and such circuit are known as series circuits.



(a) Series circuit. (b) Equivalent circuit.

Let these resistors R_1, R_2 and R_3 be connected in series across a battery.

As V acts as shown in fig. (a).

Obviously this p.d. across causes the flow of current of I amp. throughout all the resistors R_1, R_2 and R_3 . Now according to Ohm's law, Voltage drop across resi. R_1 , $V_1 = IR_1$

Voltage drop across resi. R_2 , $V_2 = IR_2$

Voltage drop across resi. $R_3 = IR_3$

Now, Voltage drop across whole ckt,

$$V = IR_1 + IR_2 + IR_3 = I(R_1 + R_2 + R_3)$$

$$\text{or } \frac{V}{I} = R_1 + R_2 + R_3$$

According to Ohm's law the ratio V/I is R .


$$R = R_1 + R_2 + R_3 \quad (1)$$

Thus, when no. of resistances are connected in series, the equivalent resistance is given by the individual resistances.

$$\text{i.e. } R = R_1 + R_2 + \dots + R_n$$

$$\text{or } R = \sum_{i=1}^n R_i$$

Voltage division in series circuit:-

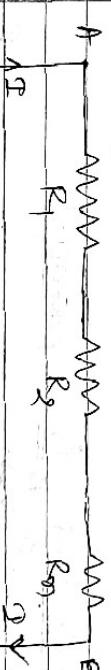

Let 'n' resistances R_1, R_2, \dots, R_n be connected in series across a battery of I amp. Volts as shown in fig. The current flowing through all the resistances I and is same as shown in fig.

The equivalent of total resistance,

$$R = R_1 + R_2 + \dots + R_m = \frac{V}{I} - (1)$$

\Rightarrow According to ohm's law, the current flowing in the series ckt, $I = V/R$ — (2)

\Rightarrow Voltage drop across each resi. is $V_1 = I R_1$ $V_2 = I R_2$ \dots $V_m = I R_m$ — (3)

∴ we get, $V_1 = V/R$ $R_1 = V/V_1$


$$V_2 = \frac{V}{R} R_2 = \frac{R_2 V}{R}$$

$$V_m = \frac{V}{R} R_m = \frac{R_m V}{R} \quad (4)$$

∴ Voltage drop across any resistance R_x in the series circuit,

$$V_x = \frac{R_x}{R} V \quad (5)$$

* Resistances in parallel:-

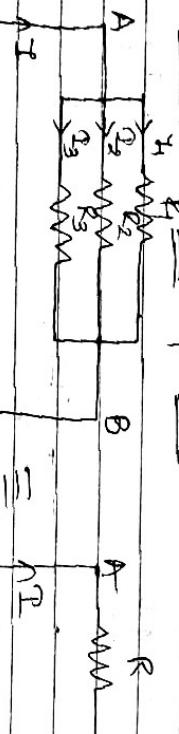

$$\text{Since } I = I_1 + I_2 + I_3 = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] \quad (1)$$

$$\therefore I = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] \quad (2)$$

$$\text{or } \frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (3)$$

$$\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (4)$$

(a) R_{eq} connected in parallel (b) Equiv. circuit

\Rightarrow If three resistances R_1, R_2 and R_3 be connected in parallel as shown in fig.

and the p.d. of V volts be applied across the circuit. The total current I divides into three parts $- I_1$ flowing through R_1 and I_2 flowing through R_2 and I_3 flowing through R_3 . Since the potential difference across each resi. is same and equal to the p.d. applied to the parallel circuit i.e. V volts


\Rightarrow According to ohm's law, $R_1, I_1 = \frac{V}{R_1}$ — (1)

$$\text{current in resi. } R_2, I_2 = \frac{V}{R_2} \quad (2)$$

$$\text{current in resi. } R_3, I_3 = \frac{V}{R_3} \quad (3)$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_m} \quad (6)$$

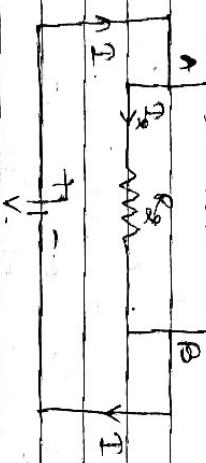* Division of current in parallel circuit.



\Rightarrow Fig. shows two resistances having

resistances R_1 and R_2 connected in

parallel across a supply voltage of V volts. Let the current in each

branch be I_1 and I_2 respectively.

\Rightarrow According to Ohm's law,

$$I_1 = \frac{V}{R_1}$$

and current flowing through resi. R_2 ,

$$I_2 = \frac{V}{R_2} \quad (P)$$

From eqn's (P) & (P)

$$V = I_1 R_1 = I_2 R_2 \quad (PP)$$

$$I_1 R_1 = I_2 R_2$$

$$\frac{I_1}{R_1} = \frac{I_2}{R_2} \quad (PV)$$

\Rightarrow It is obvious that

$$I = I_1 + I_2 \quad (V)$$

$$\Rightarrow I_2 = I - I_1$$


$$\text{get, } \frac{I_2}{I - I_1} = \frac{R_2}{R_1}$$

$$\therefore I_2 R_2 = R_1 (I - I_1)$$

$$\therefore I_2 = \frac{R_1}{R_1 + R_2} I$$

$$\text{Similarly, } I_2 = \frac{R_1}{R_1 + R_2} I \quad (P)$$

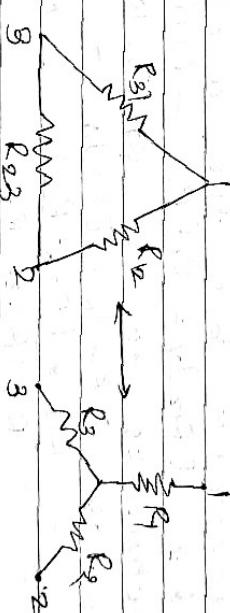Delta-star and star-Delta Transformation:



(P) (P)

\Rightarrow Consider a configuration shown in fig. (P).

where these three resistances R_{12} , R_{23} and R_{13} are connected in delta between the terminals 1, 2 and 3. So bas als the respective

terminals are connected, these three given resistances can be replaced by three resistances R_1 , R_2 and R_3 connected in star as shown in fig. (P).

\Rightarrow These two arrangements will be electrically

equivalent is the resistance as measured between any pair of terminals is the same for both the arrangements i.e. $[R_{12}]_Y = [R_{12}]_A - \text{c.f.}$

* First consider delta connection:
 \Rightarrow Between terminals 1 and 2, there are

parallel paths; one having a resistance of R_2 and the other having a resistance of $(R_3 + R_4)$.

$$R_{12} \times (R_{23} + R_{31})$$

Equations (12) to (3) are the formulas base della stessa trasformazione.

Subtraction of eqn (iv) from eqn (ii) gives

Now consider stage connection:
 The resistance bet' the same terminals
 has 1 & 2 $[R_{12}]_4 = R_1 + R_2 - [C_{11}]$
 free networks to be equivalent of

$$\text{Q.E.D.} \quad R_1 + R_2 = R_{12} \star (R_{23} + R_{31}) \quad (\text{iv})$$

Similarly, for terminals 2 and 3 and 1, we get

$$R_2 + R_3 = \frac{R_{B3} x}{R_{2+R_{23}} + R_{31}} \quad (CV)$$

$$R_{2+R_3} = \frac{R_{B3} x}{R_{2+R_{23}} + R_{31}} \quad (CV)$$

No. 63

$$R_1 + R_2 + R_3 = R_{12} R_{23} + R_{23} R_{31} + R_{31} R_{12} \quad (\text{ciii})$$

Now,
 $D^P_{R_1 R_2 R_3} \text{ of eqn (11) by eqn (2) gives}$
 $R_{R_1 + R_2 R_3 + R_3 R_1} = R_{12}$

$$\therefore R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{R_1 + R_2 + R_3 R_2}{R_3} \quad (5)$$

Similarly division of eqn (4) by eqn (5) gives

$$R_{12} + R_2 R_3 + R_3 R_1 = R_{23}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{R_1 + R_2 + R_3 R_1}{R_1} \quad (6)$$

Similarly division of eqn (4) by eqn (2)

$$R_{12} + R_2 R_3 + R_3 R_1 = R_{31}$$

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} \quad (7)$$

* Kirchhoff's laws :-

(1) Kirchhoff's first law:

\Rightarrow It is also known as Kirchhoff's current law (KCL) or junction law. It

states that the algebraic sum of all currents terminating at a point is zero at any instant of time.

$$\Rightarrow \text{Mathematically } \sum_{i=1}^n I_i = 0 \quad (1)$$

where n denotes the no. of branches meeting at the point.

* Explanation: An algebraic sum is the sum which the sign of the jnt. is taken into account. If the currents entering a node are assigned five sign, then the currents leaving the

node will be assigned vice versa sign or vice versa. \Rightarrow The choice of the sign convention is arbitrary, but once a sign convention is chosen, it should not be changed.

e.g. if any particular node contains existing KCL eqn applying KCL the currents directed towards a node are considered positive and these directed away from a node are considered negative.

\Rightarrow Consider a portion of some network as shown in fig. currents I_2 and I_4 are entering the node O. Hence they are assigned +ve sign. Currents I_3 , I_5 and I_6 are leaving the node O and hence they are assigned -ve sign.

Applying KCL at node O, we get, $I_2 + I_4 + (-I_3) + (+I_5) + (-I_6) = 0$

$$\text{or } I_2 + I_4 = I_1 + I_3 + I_5 \quad (2)$$

as sum of incoming currents = sum of outgoing currents.

(2) Kirchhoff's second law:-

\Rightarrow It is also known as Kirchhoff's voltage law or mesh law.

\Rightarrow It states as follows: At any instant

at time, the algebraic sum of all branch voltages around any closed loop of a electric network is zero. In other words, the algebraic sum of volts around a closed loop is equals the algebraic sum of IR drops along the loop. This law can be mathematically stated as

$$\sum V_i = 0 \quad (3)$$

where V_i is the voltage in the i^{th} element of a closed loop having n branches.

* **Superposition Theorem:-**

\Rightarrow Statement: "In a linear network containing more than one source of voltage or current, the total current or voltage in any branch of the network is equal to the algebraic sum of the currents from all the sources acting separately by each source acting separately at a time while all other sources set to zero leaving behind the parallel resistances in the network."

* **Application:-**

\Rightarrow Select any one of energy in the circuit
 \Rightarrow Set all other independent sources equal to zero. Then is, replace all other placed voltage sources by short circuits and cut other placed current sources by open circuit.

\Rightarrow keep the dependent sources in the circuit undistributed.


\Rightarrow Determine the magnitude and direction of current through the desired branch as a result of a single source selected in step 1.

\Rightarrow Repeat steps 1 to 4 for each source in turn until the component currents through the desired branch has been calculated due to each and every source acting alone at a time.

\Rightarrow Algebraically add all the component currents to obtain the desired branch current. This sum is the actual current through all sources are acting simultaneously i.e. when all sources are present.

* **Thevenin's Theorem:-**

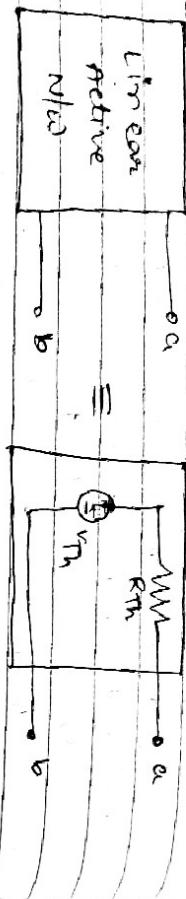Statement: Any linear, active, balanced w/o consisting of independent voltages and current sources and resistors, can be



(a) Linear Active


Netwerk Valerij Wetterskip

replaced at a point on terminals of
by a simple equivalent network

consisting of a single voltage source V_m in series with a single resistance R_m as shown in fig. (b). The single voltage source V_m is the voltage

class the terminals at which they are open excited. This voltage is called the Thevenin equivalent voltage. V_{TH} . The series resistance R_{TH} is given by the ratio of open circuit voltage V_{TH} and the short circuit current I_s . The current I_s is the current at the original meter mark. That is,

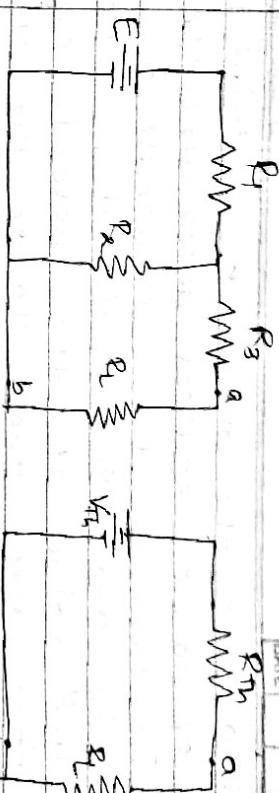* Application:-
⇒ Remove the resistance R thus creating an open circuit at terminals $a-b$.
With respect to voltmeter, the Thevenin equivalent network is designed.



(b) Thevenin's Equ. w/o

(a) Network
 Find the voltage across the terminals
 when they are open circuited.
 This voltage is called Thevenin voltage
 V_{th} or V_o

(b) Thevenin's Equ. in
 $V_o = \frac{R_o}{R_o + R_s} V_s$

\Rightarrow (i) If all the resistances sources in the circuit are independent, the equivalent resistance R_{th} is equal to the total resistance at open circuit terminals a-b, i.e., looking back from a-b across our ideal voltage source we get

by short circuits and our ideal voltage sources are replaced by open circuit terminals a-b, then independent sources are replaced by their terminal resistance.

\Rightarrow In fig. (a), short circuit the battery and find the R_{th} of the network as seen from the terminals a-b.

$R_{th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$ ————— (i).

(iii) In case the network contains the dependent sources determine the current through the terminals A-B when they are short-circuited. Determine the value of the Thvenin resistance R_{Th} with the help of the relation

$$R_{Th} = \frac{V_{Th}}{I_{sc}}$$

\Rightarrow Draw the Thvenin's equivalent "between" the terminals A-B by connecting the voltage source V_{Th} in series with R_{Th} as shown in fig. (b).


In step 1 is noted the connected across the terminals A-B. It is to be noted that the polarity of V_{Th} is such that it produces the current in the resistance R_{Th} in the same direction as the original network produced it.

In fig. (a), the current through R_{Th} is

$$I_{sc} = \frac{V_{Th}}{R_{Th}}$$

* Norton's Theorem:

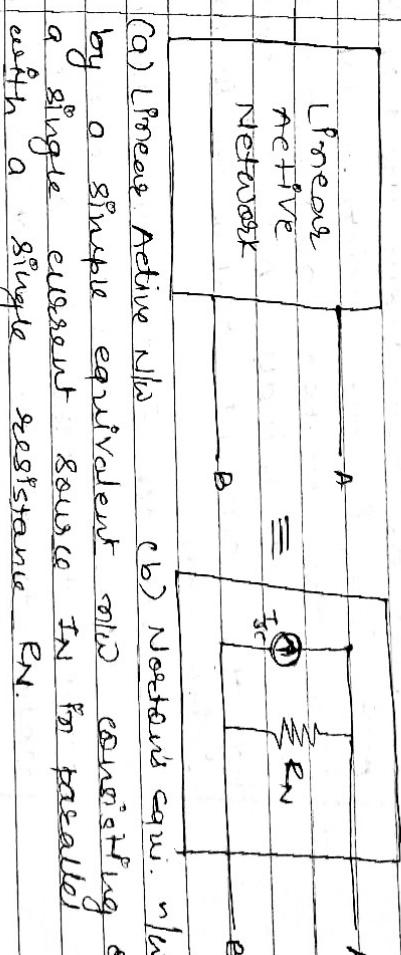\Rightarrow statement: Any linear, active, bilateral network consisting of voltage and current sources and resistors, can be replaced by a pair of terminals A-B



(a) Linear Active Netw. by a single current source in parallel with a single resistance R_N .

* Application:-

\Rightarrow Remove the resistance R_L , thus creating an open circuit between terminals A and B. Short circuit the terminals A and B w.r.t. which the Norton equivalent network is desired.

\Rightarrow Determine the short circuit current at these terminals. This current is known as I_{sc} . This is an alternative method of determining I_N from the following relation:

$$I_N = \frac{V_{Th}}{R_{Th}}$$

\Rightarrow Redraw the network with each ideal voltage source replaced by a short circuit and each ideal current source replaced by an open circuit. Non-ideal sources are replaced by their internal resistance

metre-peak as seen from the terminals.

A-B. This is the resistance law.

at the terminals A-B by connecting the current source in parallel

→ The resistance R_1 that was removed

across the terminals A-B. It is to be noted that the direction of IN is such that it circulates the current from the resistance R for the same direction as the original current experienced it.

The different Haemagglutinin's is calculated from the haemagglutination dilution rule.

卷之三

\Rightarrow Maximum power transfer theorem:
Statement: A satisfactory load condition

Stockmen in Mrs. STRIVE's
to a d. c. George York comes way. However

concern the load resistance is equal

\Rightarrow To the second resistance. i.e. $H =$

prosternal resistance. Res. It is supporting a cossent to a Nasalate load 20g.

\Rightarrow The load current is

$$\frac{R_s + R}{E} = \text{frac by } \text{given}$$

The process delivered

$$P = \frac{I^2}{R}$$

四


at P to

$$\text{d}P = \frac{1}{E^2}$$

$$(R_3 + R_L) - \alpha R_L (R_3 + R_L) = 0$$

$$R_c = R_s \quad (2)$$

DP should be

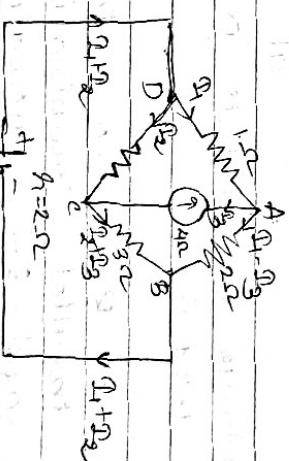

\Rightarrow Applying KVL to the closed path DABED.

$$-I_1 - 4I_3 + 2I_2 = 0 \quad \text{--- (i)}$$

Similarly, for closed path ABCAC we get

$$2I_4 - 3I_2 + 3(I_2 + I_3) + 4I_3 = 0 \quad \text{--- (ii)}$$

$$2I_4 - 3I_2 - 9I_3 = 0 \quad \text{--- (iii)}$$

$$\text{Similarly, for closed path DABED, we get} \\ -I_1 - 2(I_2 + I_3) - 2(I_2 + I_4) + 2 = 0 \\ 5I_4 + 2I_2 - 2I_3 = 2 \quad \text{--- (iv)}$$

Writing above eq's in matrix form,

$$\begin{bmatrix} 1 & -2 & 4 & 0 \\ 2 & -3 & -9 & 0 \\ 5 & 4 & -2 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 2 \end{bmatrix}$$

Using cramer's rule.

$$I_1 = \frac{30}{q_1}, \quad I_2 = \frac{q_1}{q_1} \text{ A and } I_3 = \frac{1}{q_1} \text{ A}$$


$$\Rightarrow P.D. \text{ across D and B} = 2 - 2 \left(\frac{30}{q_1} + \frac{1}{q_1} \right)$$

$$\Rightarrow \text{equi. resistance bet' points D and B} = \frac{2}{q_1} \text{ V}$$

$$\Rightarrow \text{equi. resistance bet' points D and B} = \frac{2}{q_1} = 1.87 \Omega$$

$$= 4791$$

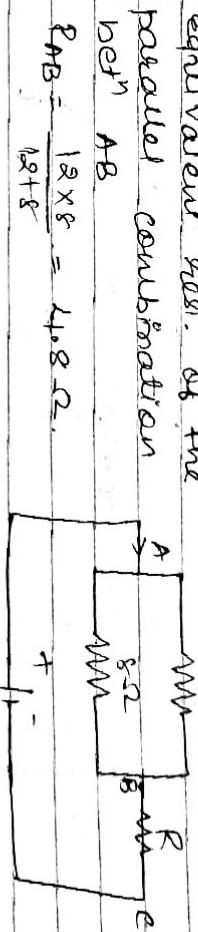Ex: A resistance R is connected to series with a parallel combination of two res. 12Ω and 8Ω . Calculate R if the



\Rightarrow From eq (i) & (ii), we get
 $R + 4.8 = 5.44 \therefore R = 0.914 \Omega$

Ex: Determine the current supplied by the source in the circuit at $t = 0$.

Total resistance of the circuit $= \frac{V}{I} = \frac{20}{2.5} = 8 \Omega$

power dissipated in the circuit $= P = 70W$

D.P. across the circuit $V = 20V$


current through the circuit $I = \frac{P}{V} = \frac{70}{20} = 3.5A$

total resistance of the circuit $= \frac{V}{I} = \frac{20}{3.5} = 5.714 \Omega$

$$\text{Resistance bet' A & C} = \frac{4 \times 4}{4+4} = 2 \Omega$$

\Rightarrow Since partly the resistance both are
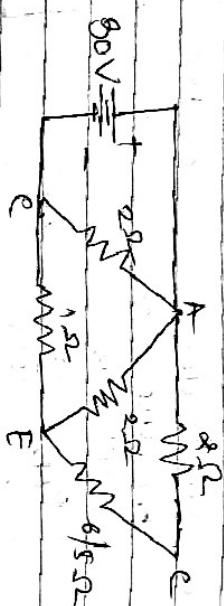
$$= \frac{g}{1} \times (2+1) = \frac{g \times 3}{1} = \frac{6}{1} \text{ N}$$



New resistance belt

$$= 2 \cdot \frac{1}{1} \left(\frac{a+b}{5} \right) = 2 \cdot \frac{1}{1} \frac{16}{5} = \frac{16}{5} = 3 \frac{1}{5}$$


Res. betw A & E

$$= \frac{1}{2} \left(1 + \frac{1}{3} \right) = \frac{2}{3}$$

expenses supplied by people

$$I = \frac{30}{-1} \rightarrow 30.14 \text{ Amp}$$

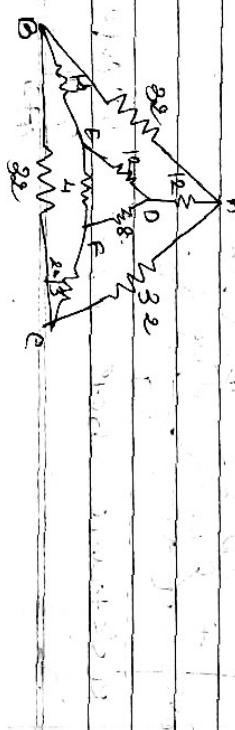(5) The network shown in fig., determine the resistance bet' A and B. The resistors represent the 'respective resi. in ohms.




PAGE NO.

$$E_1 = 12 \times 8 = 48$$

20
+ 3
—
23

The diagram shows a three-phase star (Y) connection. The top vertex is labeled 'O'. The bottom-left vertex is labeled 'E' and the bottom-right vertex is labeled 'D'. Phase currents I_1 , I_2 , and I_3 flow downwards through resistors R_1 , R_2 , and R_3 respectively. Inductor L_1 is connected between phase I_1 and the common neutral point 'O'.


$$R_3 = 25\Omega$$

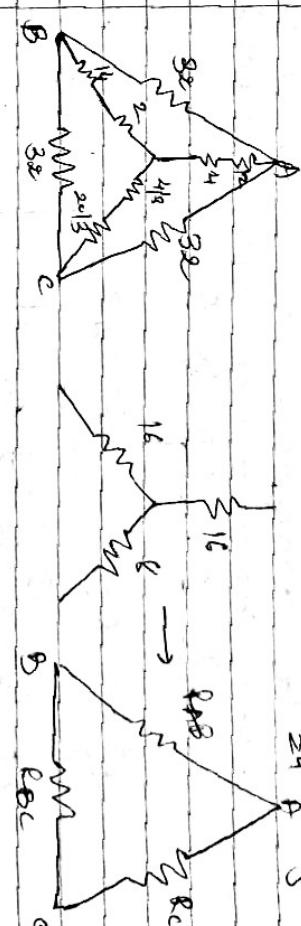

$$P_{AB} = 16 + 16 + 16 \times 16 = 64 \text{ or } P_{BC} = 16 + 5 + 16 \times 5$$

$$ReA = \frac{16 + 8 + 16 \times 8}{16} = 32.5$$

elegans


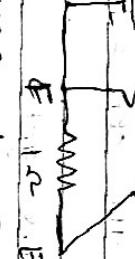


PAGE NO.
DATE

\Rightarrow Effective resi. bet' terminals A-B.

$$= \frac{64}{3} \parallel (18+16) = \frac{64}{3} \parallel 16.8\Omega = 12.8\Omega$$

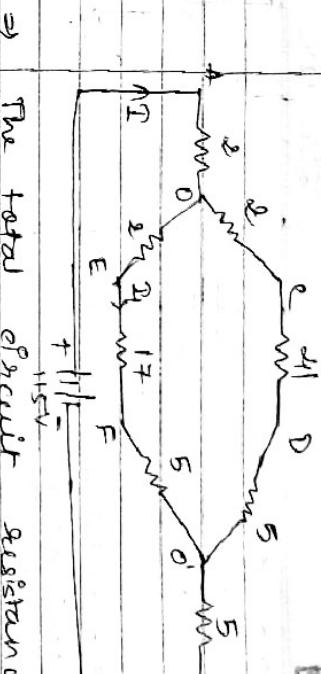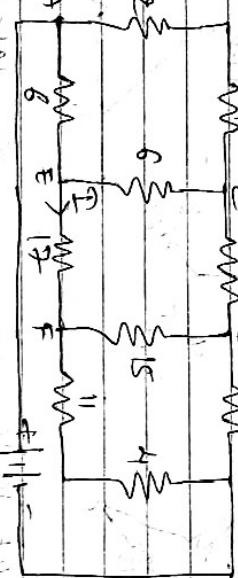* Find the current in 17Ω resistor in the network shown fig. using star delta connection. The numbers indicate the resistance of each member in ohms.



\Rightarrow The total circuit resistance

$$R = 2 + 5 + (2 + 4 + 15) \parallel (2 + 12 + 5)$$

$$= 2 + 5 + (48) \parallel 11.24 = 2 + 5 + 16 = 23\Omega$$

current supplied by the supply

$$I = \frac{V}{R} = \frac{12}{23} = 0.53A$$

\Rightarrow Current in 17Ω resi, $I_1 = 0.5 \times \frac{45}{45+24}$


$$= 0.5 \times \frac{45}{69}$$

Ex:


Find the current in the 10Ω resis. of the circuit shown in fig. Use

meshes

or
KVL theorem. Given $12V$

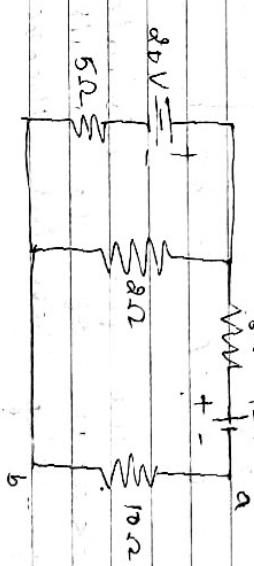

\Rightarrow Determination of V_{BD}

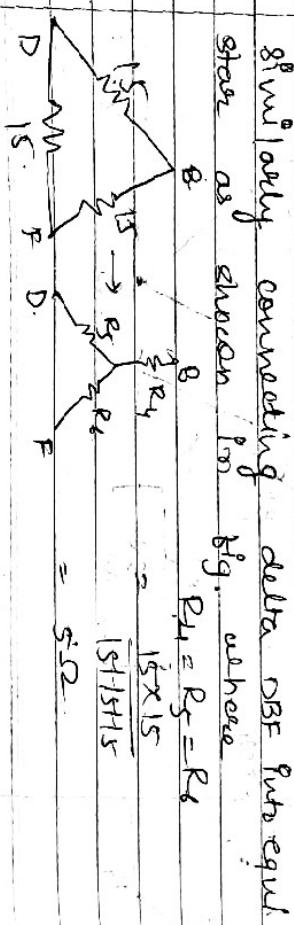

\Rightarrow Star delta connecting delta DBF into equal shear as shown in fig. where

$$R_1 = R_2 = R_3 = \frac{15 \times 15}{15+15+15}$$

$$R_1 = R_2 = R_3 = \frac{6 \times 6}{6+6+6} = 2\Omega$$

\Rightarrow Star delta connecting delta DBF into equal shear as shown in fig. where

$$R_1 = R_2 = R_3 = \frac{15 \times 15}{15+15+15}$$

\Rightarrow Determination of V_{BD}

PAGE NO.	12
DATE	12/12/19
TIME	10:45 AM

PAGE NO.	12
DATE	
TIME	


$$V_{ab} = 20 \times \frac{8}{2+5}$$

$$= 40 \text{ V.}$$

\Rightarrow

$$\text{Now, } V_{th} = V_{ab} - V_{cb}$$

$$= 12 + \frac{40}{7}$$

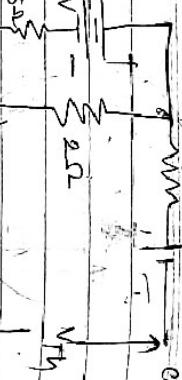

$$= -6.2857 \text{ V.}$$


i.e. the point b is at higher potential

$$(i) \text{ Determination of } R_{Th}:$$

$$\Rightarrow R_{Th} = 8 + (2+5)$$

$$= 8 + \frac{10}{7}$$

$$= 9.4286 \Omega.$$

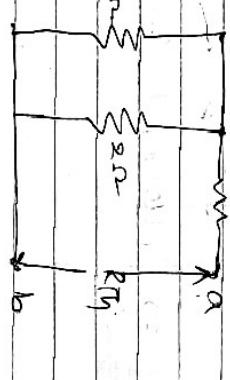


\Rightarrow Connecting 4A current source from voltage source and removing the 10Ω resistance the cur. is shown in fig.

current in 15Ω resis. = $\frac{80-20}{15+5+1} = \frac{55}{21} \text{ A.}$

$V_{th} = 2 + \frac{55}{21} \times 1 = 4.762 \text{ V.}$

$R_{Th} = 1/(15+5) = 0.9524 \Omega.$

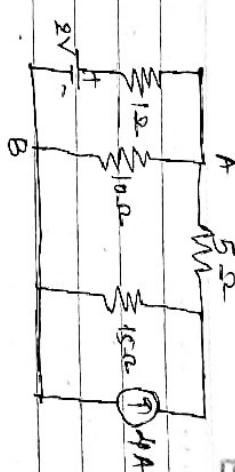

(ii) Thévenin's eqn: $V_{th} = 9.4286 \Omega$

$$\Rightarrow V_{th} = R_{th} + R_L$$

$$= 9.4286 + 10$$

$$= 0.3235 \Omega \text{ (open loop).}$$


Ex: Find the power dissipated in the 10Ω resistor of the circuit shown in fig. using Thévenin's theorem.

Ans: Power in 10Ω resistance = $I^2 R_L$

Power in 10Ω resistance = $(0.4348)^2 \times 10$

= 1.89 W.

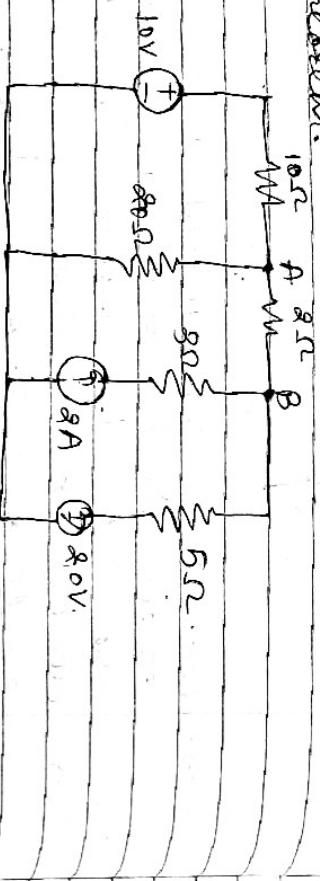Ex: Find the voltage across the $\frac{1}{2}\Omega$ resistor by using the superposition theorem.



Let us find the voltage across the $\frac{1}{2}\Omega$ resistor due to individual sources. The algebraic sum of these voltages gives the total voltage across the $\frac{1}{2}\Omega$ resistor.

Step 1: consider 10V source.

Assume a voltage V at node A. Applying KCL we get

$$10V = \frac{V}{2} + \frac{V-10}{\frac{1}{2}} + \frac{V-10}{10}$$

$$\therefore V[0.1 + 0.05 + 0.143] = 10$$


$$\therefore V = 3.41V$$

$$10V = \frac{3.41}{2} + \frac{3.41-10}{\frac{1}{2}} + \frac{3.41-10}{10}$$

$$\therefore V = 3.41V$$

The voltage across $\frac{1}{2}\Omega$ resistor due to 10V source is $V_1 = 3.41 \times \frac{1}{2} = 0.97V$

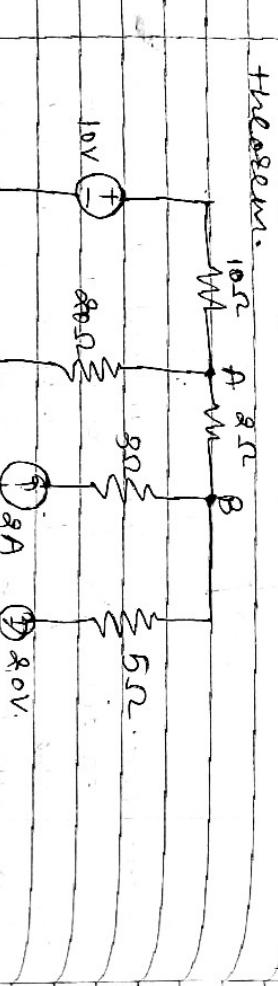Step 2: consider 2A source to find the voltage across $\frac{1}{2}\Omega$ resistor while the other sources are set to zero.




∴ the voltage across the $\frac{1}{2}\Omega$ resistor due to 20V source is

$$V_2 = \left(\frac{20-V}{\frac{1}{2}} \right) \times \frac{1}{2}$$

$$= 2 \cdot 9.42V \quad (\text{opposite polarity})$$

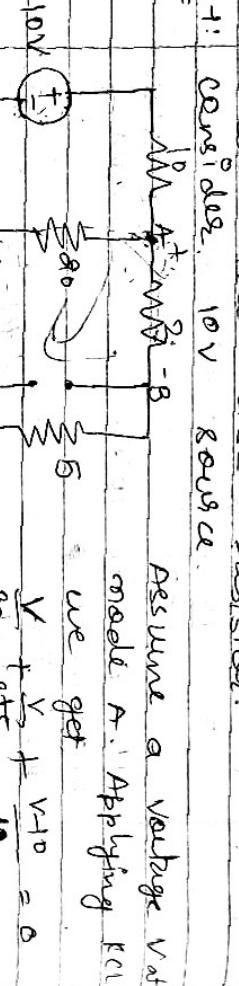Step 3: consider 2A source to find the voltage across $\frac{1}{2}\Omega$ resistor while the other sources are set equal to zero.



The voltage across $\frac{1}{2}\Omega$ resistor is $V_3 = 2 \times 0.73 = 1.46V$ (opposite polarity)

Applying superposition theorem

$$V_{AB} = V_1 + V_2 + V_3 = 0.97 - 2.92 - 1.46$$

$$= -3.41V \quad (B \rightarrow A)$$




Ex: Determine the current through the $\frac{1}{2}\Omega$ resistor of fig. by using Norton's theorem.

Assuming voltage V at node A as shown in fig. The KCL eqn is

$$\frac{V-20}{\frac{1}{2}} + \frac{V}{2} + \frac{V}{10} = 0.$$

$$\frac{V}{2} + \frac{V}{2} + \frac{V}{10} = 20$$

$$V = 20V$$

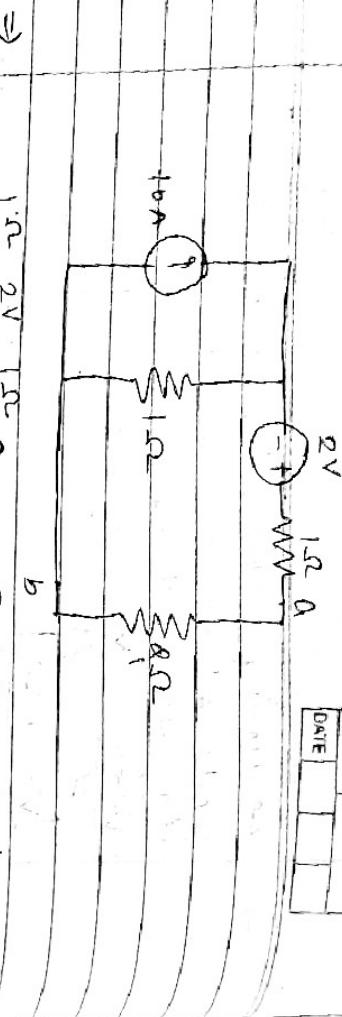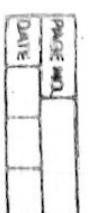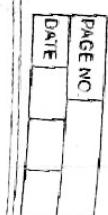

across the terminals and as shown
by fig.
In fig., by current
division rule.

$$T = \frac{2}{2+2} \rightarrow x 6$$


$= 3A.$

Current through α

resistor = $3A.$

Ex: for the network shown in fig. draw

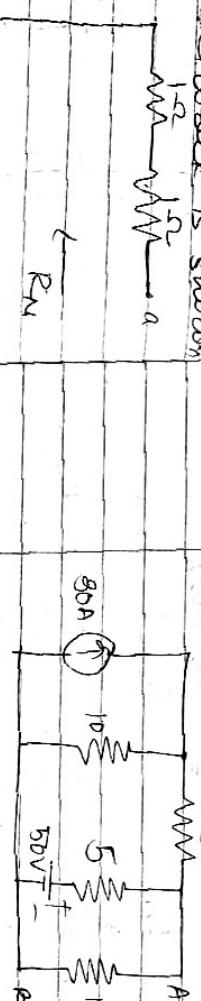No two equivalent metronomes and determine the current throughout 15Ω resistors. All resistances are from Burns



卷之三

\Rightarrow Since there are two sources due to which current will flow between A and B. Therefore applying superposition

Considering only current source, the
crt. is reduced as shown in fig.


\Rightarrow Considering only voltage source, the current will be as shown in fig.

below.

From the fig.

$$I_L = \frac{50}{5}$$

$$= 10 \text{ Amp.}$$

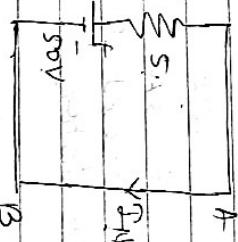

\Rightarrow According to superposition theorem, Norton current $I_N = I_{N1} + I_{N2}$

$$= 80 + 10$$

$$= 30 \text{ Amp.}$$

\Rightarrow To calculate the R_N , the ext. is removed between the terminals A and B and shorted to zero.

$$\therefore R_N = \frac{5}{5+10}$$

$$= 0.45 \Omega$$

\Rightarrow Norton equivalent w/o


is shown in fig.

$$\text{through } 15 \Omega \text{ resistor, } R = 30 \times \frac{3.75}{8.75+15}$$

$$= 8.15 \Omega$$

$$= 6 \text{ Amp.}$$

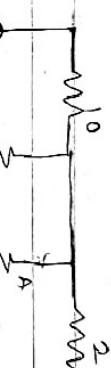Ex: Determine the current flowing through the 5 Ω resistor in the circuit of fig. using Norton's theorem.



$$\Rightarrow I_N = 30 \text{ Amp.}$$

$$R_N = 5 \parallel (2+1)$$

$$= 5 \parallel (2 + \frac{1 \times 2}{1+2})$$

$$= 5 \parallel 2.5$$

$$= \frac{5 \times 2.5}{5+2.5}$$


$$= 1.67 \Omega$$

$$\Rightarrow \text{Norton's equiv. ext.}$$

$$\Rightarrow \text{current through } 5 \Omega \text{ res.}$$

$$I_L = 30 \times \frac{1.67}{1.67+5}$$


$$= 4.5 \text{ A.}$$

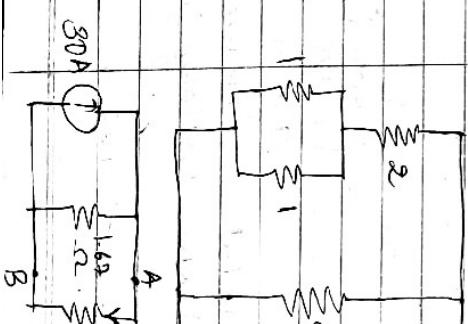

Ex: Fig. shows a circuit feeding a load R_L . Find the value of R_L so that current supplied by battery = 4A.

(a) when R_L is adjusted to max.

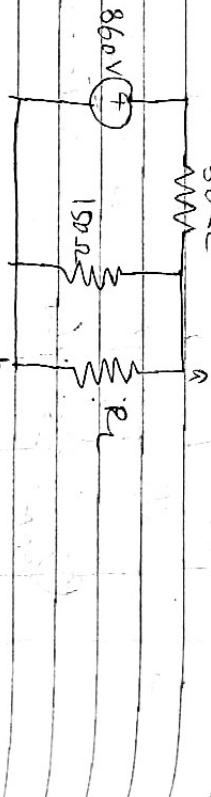(b) when R_L is adjusted to min. calculate this power delivered by the battery.



$$(a) \Rightarrow V_{th} = 860 \times \frac{150}{150+30} = 800V$$

$$R_{th} = 80 || 150 = 85\Omega$$

\Rightarrow Thevenin's equl. v/lw is shown in fig. For max. power transfer R_L should be equal to R_{th} .

$$\text{i.e. } R_L = R_{th} = 85\Omega$$

$$\text{Power delivered to load} = P_{RL}$$

$$= \left(\frac{800}{85+85} \right)^2 \times 85$$

$$= 900W$$

(b) when $R_L = 85\Omega$, the total resistance at the vlt. as seen from battery terminals

$$= (80 + 85) || 150$$

$$= \frac{30 + 85 \times 150}{85 + 150} = 31.428\Omega$$

$$\text{Power supplied by battery} = 860 \times 4 = 3440W$$

$$\text{Percentage of power delivered to the load} = \frac{900}{3440} \times 100 = 35.4\%$$

Ch. 8 Work, Power and Energy

* Work: Work is said to be done by a force when it moves a body through a certain distance. It is measured for tensing of the string or the spring and the distance moved in the direction of the force.

$$\text{Work} = \text{Force} \times \text{distance}$$

$$W = F \times d$$

$$1 \text{N m} = 1 \text{J}$$

* Power: Power is defined as the rate of doing work or the amount of work done in unit time.

$$\text{i.e. Power} = \frac{\text{Work}}{\text{Time}}$$

$$\text{Mathematically } P = \frac{W}{t}$$

$$1 \text{ watt} = 1 \text{ joule/second}$$